



```
import matplotlib.pyplot as plt
from math import *
R = 1.0
L = 1.0
V \text{ out } = R
V_ratio = []
frequency = []
w = 1.0
dw = 0.1
w_final = 100.0
t = 1.0
dt = 0.1
t_f = 100.0
#for plot of ratio vs. frequency
#this is a low frequency filter
while w < w_final:</pre>
         V_{in} = sqrt(R^{**}2+(w^*L)^{**}2)
         v_ratio = V_out/V_in
         V_ratio.append(v_ratio)
         frequency.append(w)
         w = w + dw
k = 1.0
dk = 1.0
k_f = 100.0
V_In = []
V_Out = []
Time = []
shift = pi
#for new Vin that is a square wave
       t < t_f:
         k = 1.0
         V_{in} = 0.0
         V_{out} = 0.0
               k < k_f:
                  V_{in} = V_{in} + ((4.0/pi)*(sin(((2.0*k)-1.0)*w*t))/((2.0*k)-1.0))
                  V_{\text{out}} = V_{\text{out}} + ((4.0/\text{pi})*(\sin((((2.0*k)-1.0)*w*t)+ \text{shift}))/
((2.0*k)-1.0)
                  #I am not sure how the output voltage changes but I think that it is
jut going to be more like a sine wave (edges will be smoother)
                  k = k + dk
         Time.append(t)
         V_In.append(V_in)
         V_Out.append(V_out)
         t = t + dt
#plt.plot(frequency,V_ratio)
#plt.ylabel(r"\frac{V}{IN}{V {OUT}}$", fontsize =12)
#plt.xlabel('Frequency (1/s)')
#plt.title('Voltage Ratio vs. Frequency')
```

```
plt.plot(Time, V_In, label='Input voltage')
#plt.plot(Time, V_Out, label='Output Voltage')
plt.xlabel('Time (s)')
plt.ylim(-3,3)
plt.ylabel('Input Voltage')
plt.title('Input Voltage as a function of time')
plt.legend()
plt.show()
```